

SIR ARTHUR LEWIS COMMUNITY COLLEGE
ENGINEERING AND THE CIRCULAR ECONOMY
ACADEMIC YEAR (2024/2025) - SEMESTER ONE
END OF SEMESTER EXAMINATION

TUTOR (S) : Mr. Kendall Numa

PROGRAMME TITLE : Computer Systems Engineering

COURSE TITLE : Electricity

COURSE CODE : ELE112

LEVEL : Associate Degree/ Year One

PAPER : One

DATE : Thursday, 12th December 2024

COMMENCEMENT TIME : 1:00 p.m.

DURATION : Two (2) Hours

INVIGILATOR(S) : D. Jn Baptiste, A. Mason, A. L-Goodman,
M. St Clair, A. Regis

ROOM(S) : LFT-1R-05

GENERAL INFORMATION AND INSTRUCTIONS

- This paper consist of Two (2) Sections (A and B). Answer the questions on the foolscap provided.
- **Section A** consist of Three (3) Long Answer Questions. You are required to **answer ALL questions**. Marks are awarded accordingly.
- **Section B** consist of Three (3) questions. You are required to **answer Only One question**. **Marks are awarded accordingly**.
- Students must sign **IN** and **OUT** on the examination class list.
- Students must **not** write their names on their answer sheets, only their ID number
- Please number your responses accurately.
- **Note: Bags, Books as well as writing paper not given by the invigilator should be deposited at the front of the examination room or as otherwise indicated.**
- **All cell phones must be turned off during the exam**

**DO NOT TURN THIS COVER SHEET UNTIL
YOU ARE TOLD TO DO SO!!!**

SECTION A

Answer ALL questions.

1. A coil of 400 turns is wound uniformly over a mild steel ring of relative permeability 70, having a mean circumference of 200 mm and a uniform cross-sectional area of 300 mm². If the current through the coil is 2 A, calculate:
- a. the magnetic field strength [2]
 - b. the magnetic flux density [2]
 - c. the total flux [2]
 - d. the reluctance of the ring [2]

[8 marks]


2. A parallel plate capacitor has 7 plates, separated by sheets of mica of thickness 0.25 mm and relative permittivity 6. The area of one side of each plate is 300 cm². If a potential difference of 400 V is maintained across the terminals of the capacitor, calculate:
- a. the capacitance [2]
 - b. the charge [2]
 - c. the electric field strength [2]
 - d. the electric flux density [2]
 - e. the energy stored in the capacitor [2]

[10 marks]

3. A coil of resistance 36 Ω and inductance 0.6 H is connected in series with a 9.4 μF capacitor. The circuit is connected to a 12 V, 70 Hz supply. Calculate:
- a. the inductive reactance [2]
 - b. the capacitive reactance [2]
 - c. the total impedance [2]
 - d. the total current [2]
 - e. the impedance of the coil [2]
 - f. the voltage drop across the coil [2]
 - g. the voltage drop across the capacitor [2]
 - h. the phase angle [2]

[16 marks]

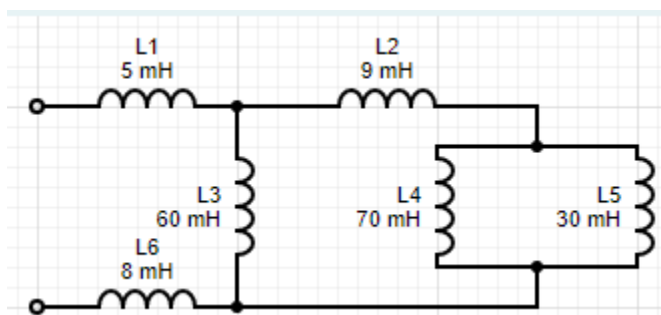4. Calculate the total inductance for the circuit shown below



[8 marks]

[TOTAL 42 MARKS]

SECTION B

Answer Only One question.


1. A resistance of $200\ \Omega$ and a pure inductance of $200\ \text{mH}$ are connected in parallel across a $100\ \text{V}$, $50\ \text{Hz}$ supply, calculate:
 - a. the inductive reactance [2]
 - b. the current flowing through the resistor [2]
 - c. the current flowing through the inductor [2]
 - d. the total current [2]
 - e. the impedance [2]
 - f. the phase angle [2]

[12 marks]

2. a. Draw a simple diagram of a transformer, naming the relevant parts [4]
- b. Explain the operation of a simple transformer [4]
- c. An ideal transformer has a turns ratio of $8:1$ and the primary current is $3\ \text{A}$ when it is supplied at $240\ \text{V}$. Calculate the secondary voltage and current. [4]

[12 marks]

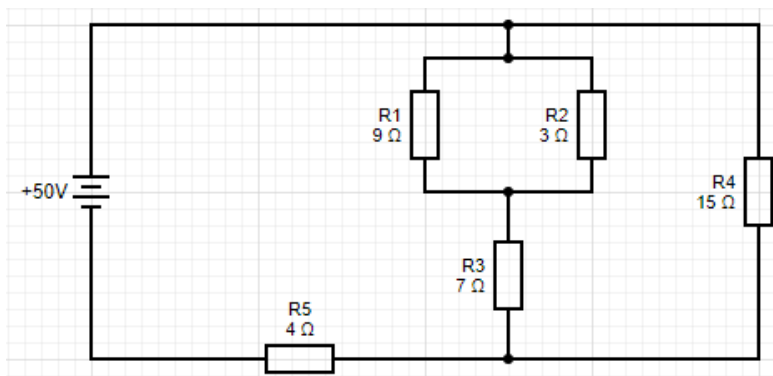3. For the circuit shown below, calculate:
 - a. the total resistance [8]
 - b. the voltage across R_4 [2]
 - c. the current flowing through R_3 [2]



[12 marks]

[TOTAL 36 MARKS]

END OF EXAMINATION!!!