

SIR ARTHUR LEWIS COMMUNITY COLLEGE
ENGINEERING AND THE CIRCULAR ECONOMY
ACADEMIC YEAR (2024/2025) - SEMESTER ONE

END OF SEMESTER EXAMINATION

TUTOR (S)	:	Mr Lindsley Philbert
PROGRAMME TITLE	:	Electrical Engineering
COURSE TITLE	:	Electronics II
COURSE CODE	:	ELE201
LEVEL	:	Associate Degree/Year One
PAPER	:	One
DATE	:	Tuesday, 10 th December 2024
COMMENCEMENT TIME	:	1:00 p.m.
DURATION	:	2 Hours
INVIGILATOR(S)	:	N. Fevrier, R. Joseph, C. Gedeon, M. John, D. Alexander
ROOM(S)	:	LFT-1R-05

GENERAL INFORMATION AND INSTRUCTIONS

- This paper consists of One (1) Section with eleven (11) questions. **Students are required to answer all questions on the foolscap provided. Marks are awarded accordingly.**
- Students must sign **IN** and **OUT** on the examination class list.
- Students must **not** write their names on their answer sheets, only their ID number.
- Students are reminded to read **all** questions and instructions in each section very carefully.
- Please number your responses accordingly.
- **Note: Bags, Books as well as writing paper not given by the invigilator should be deposited at the front of the examination room or as otherwise indicated.**
- **All cell phones must be turned off during the exam.**

**DO NOT TURN THIS COVER SHEET UNTIL
YOU ARE TOLD TO DO SO!!!**

SECTION A

Answer all questions on the foolscap provided.


- 1) Sketch the block diagram of a complete power supply and briefly discuss what happens in each of the sections. **(10 marks)**

- 2) Using a dc and ac voltmeter to measure the output signal from a filter circuit, we obtain readings of 25 V dc and 1.5 V rms.
 - i. Calculate the ripple of the filter output voltage. **(3 marks)**

- 3) A dc voltage supply provides 60 V when the output is unloaded. When connected to a load, the output drops to 56 V.
 - i. Calculate the value of voltage regulation. **(3 marks)**


- 4) Calculate the ripple voltage of a full-wave rectifier with a 100 μ F filter capacitor connected to a load drawing 50 mA. **(3 marks)**

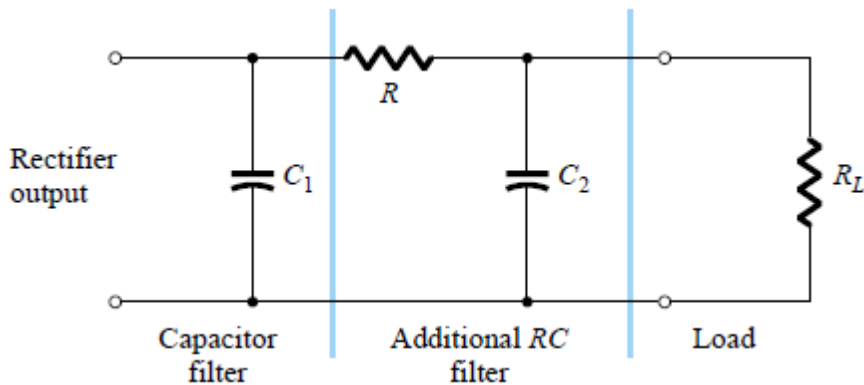- 5) Below is a circuit of a RC filter. Briefly discuss how it works. **(5 marks)**




- 6) Calculate the dc voltage across a 1-k ohm load for an RC filter section ($R = 120$ ohms, $C = 10\mu$ F). The dc voltage across the initial filter capacitor is $V_{dc} = 60$ V. **(4 marks)**

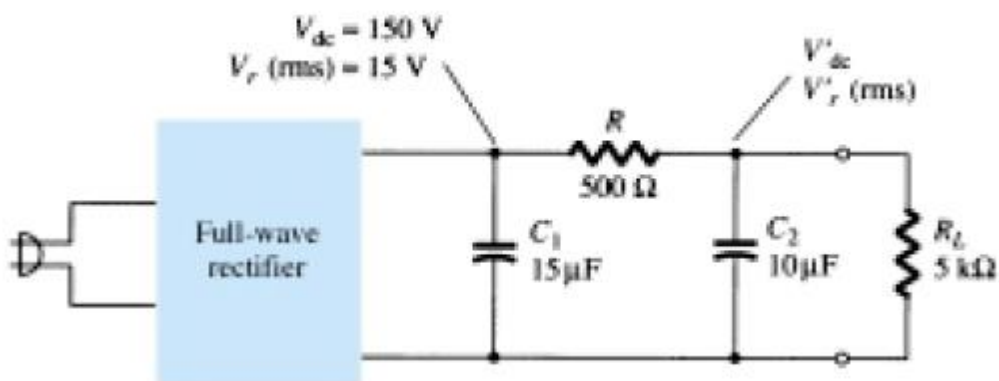- 7) Calculate the AC and DC components of the output across the load R_L in the circuit below.
 - i. Calculate the ripple of the output waveform **(6 marks)**




- 8) With a label diagram discuss the operation of a series voltage regulator **(10 marks)**

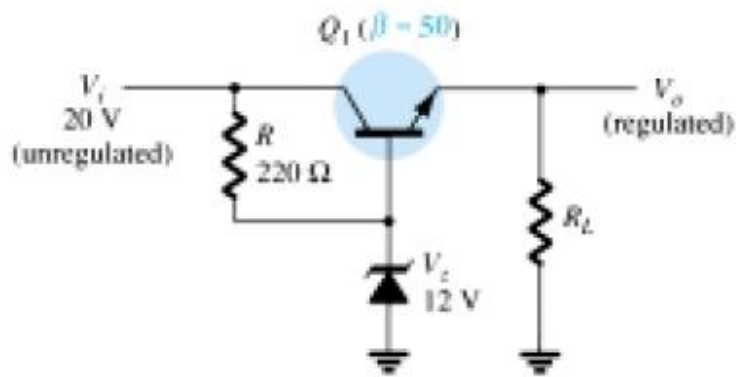
- 9) Calculate the output voltage and Zener current in the regulator circuit below. $R_L = 1$ kilo ohms (10 marks)



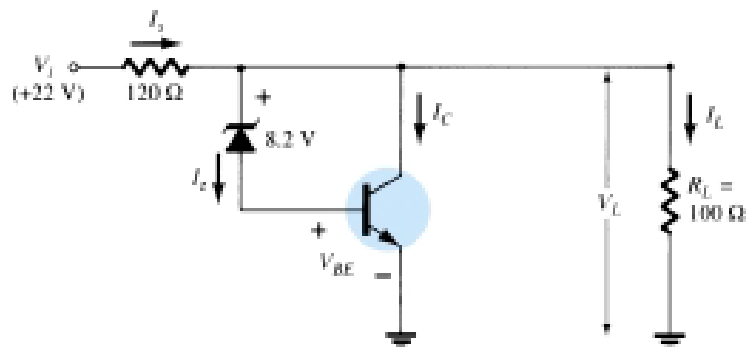- 10) Determine the regulated voltage and current for the shunt regulator below. (8 marks)



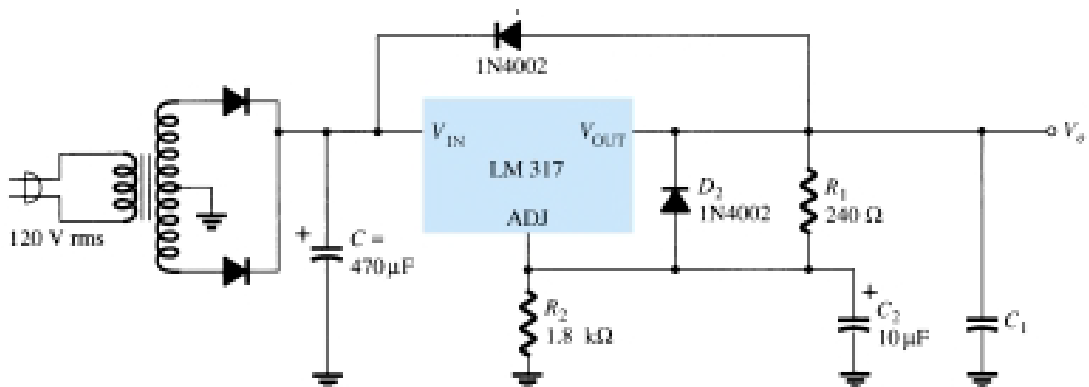- 11) Determine the regulated output voltage of the circuit below. (6 marks)



Total (68 Marks)

END OF EXAMINATION!!!