

**SIR ARTHUR LEWIS COMMUNITY COLLEGE**  
**ENGINEERING AND THE CIRCULAR ECONOMY**  
**ACADEMIC YEAR (2024/2025) - SEMESTER ONE**  
**END OF SEMESTER EXAMINATION**

**TUTOR (S)** : Mr. Kendall Numa &  
Mr. Yoany Guerra Contino

**PROGRAMME TITLE** : Computer Systems Engineering  
Electrical Engineering

**COURSE TITLE** : Digital Principles & Technology

**COURSE CODE** : ELE211

**LEVEL** : Associate Degree/ Year Twos

**PAPER** : One

**DATE** : Tuesday, 10<sup>th</sup> December 2024

**COMMENCEMENT TIME** : 9:00a.m.

**DURATION** : TWO (2) HOURS

**INVIGILATOR(S)** : T. Warner (Chief), J. E. Gaillard &  
K. O. Frederick

**ROOM(S)** : TRB-02-03

---

**GENERAL INFORMATION AND INSTRUCTIONS**

- This paper consist of Two (2) Sections A and B. Answer questions on the foolscap paper provided.
- **Section A** consist of eight (8) questions. You are required to **answer ALL questions**.
- **Section B** consist of three (3) questions. You are required to **answer ANY TWO (2) questions**.
- The number in the brackets “[ ]” next to each question are the marks allocated.
- Students must sign **IN** and **OUT** on the examination class list.
- Students must **not** write their names on their answer sheets, only their ID number
- Please number your responses accurately.
- **Note: Bags, Books as well as writing paper not given by the invigilator should be deposited at the front of the examination room or as otherwise indicated.**
- **All cell phones must be turned off during the exam**

**DO NOT TURN THIS COVER SHEET UNTIL  
YOU ARE TOLD TO DO SO!!!**

---

**SECTION A - Answer all questions**

Marks are awarded accordingly.

**Question One**


Complete the following table:

Inputs			Outputs		
A	B	C	OR	NAND	XOR
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

[3]

 **Question Two**

Sketch the Y output for the diagram shown below.



[5]

**Question Three**


Draw the **logic circuit diagram** and **truth table** for the following Boolean expression:

$$X = \overline{A\overline{B}} \cdot \overline{(A + C)} + \overline{A}B \cdot \overline{A + \overline{B} + \overline{C}}$$

[20]

 **Question Four**

Write the Boolean expression for the logic circuit diagram shown below.



[5]

**Question Five**

Simplify the following Boolean expression using the rules and theorems of Boolean Algebra

$$X = \overline{A\overline{B}} \cdot \overline{(A + C)} + \overline{A}B \cdot \overline{A + \overline{B} + \overline{C}}$$

[6]

**Question Six**

Simplify the following Boolean expression using the Karnaugh Maps Method.

$$X = \bar{A}\bar{B}\bar{C} + A\bar{C}\bar{D} + A\bar{B} + ABC\bar{D} + \bar{A}\bar{B}C$$

[4]

**Question Seven**

Write the following expression in its Boolean form

$$F(w,x,y,z)=\sum(3,7,11,13,14,15)$$

[3]

**Question Eight**

Redraw the following circuit using only NAND Gates



[4]

[TOTAL 50 MARKS]


**SECTION B – Answer Any Two Questions**

Marks are awarded accordingly.

**Question One**


(A) Draw the truth table, logic circuit diagram and logic symbol for a full adder. [6]

 (B) Determine the  $\Sigma$  and  $C_o$  outputs for the diagram shown below.



[4]

 (C) Determine the  $D_i$  and  $B_o$  outputs for the diagram shown below.



[4]


(D) Draw the block diagram of a 4 bit parallel adder using four full adders. [3]

(E) Draw the block diagram for the 7483 4-bit parallel adder IC [3]

[TOTAL 20 MARS]


**Question Two**

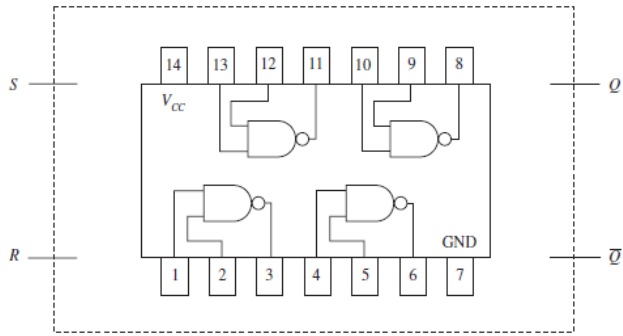- (A) Redraw the diagram below showing the connections that need to be made to the 7400 quadruple 2- input NAND gate IC to form a NAND Gate SR latch.



[4]

 - (B) Sketch the Q output for the diagram shown below.




[4]

- (C) Draw the circuit diagram for a D latch with enable using NAND Gates.


[4]

 - (D) Determine the Q output for the diagram shown below.



[4]

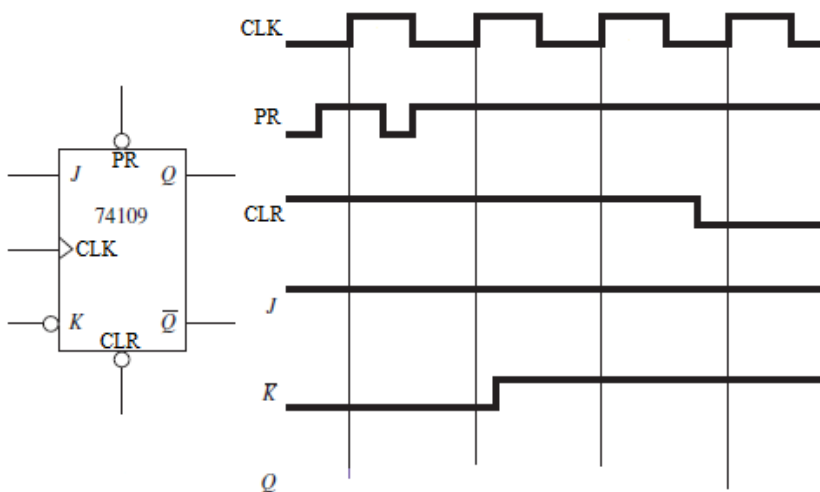- (E) Determine the Q output for the diagram shown below.



[4]

[TOTAL 20 MARKS]

### **Question Three**

- (A) Name the four classifications of shift registers and draw the 4- bit variations of any two types. [8]
- (B) Draw the circuit diagram for a ring counter. [2]
- (C) Draw the timing diagram for CLK, Q<sub>0</sub>, Q<sub>1</sub> and Q<sub>2</sub> for a 3-bit binary up counter for 10 clock pulses. [5]
- (D) Design a MOD 11 ripple up counter. [5]

**[TOTAL 20 MARKS]**

**END OF EXAM!**