

SIR ARTHUR LEWIS COMMUNITY COLLEGE
ENGINEERING AND THE CIRCULAR ECONOMY
ACADEMIC YEAR (2024/2025) - SEMESTER TWO
END OF SEMESTER EXAMINATION

LECTURER(S) : **Mr Kendall Numa**

PROGRAMME TITLE : **Computer Systems Engineering
Electronics Engineering**

COURSE TITLE : **Digital Principles & Technology**

COURSE CODE : **ELE211**

LEVEL : **Associate Degree/ Year Twos**

PAPER : **One**

DATE : **Tuesday, 6th May 2025**

COMMENCEMENT TIME : **9:00a.m.**

DURATION : **TWO (2) HOURS**

INVIGILATOR(S) : **K. Emmanuel (chief), A. Cadasse-Paul,
A Sanchez Rojo, C. Fevriere & P. Jn Francois**

ROOM(S) : **LFT-1R-05**

GENERAL INFORMATION AND INSTRUCTIONS

- This paper consist of Two (2) Sections.
- **Section A** consist of eight (8) questions. You are required to **answer ALL questions.**
- **Section B** consist of three (3) questions. You are required to **answer ANY TWO (2) questions.**
- All questions are to be attempted on the foolscap paper provided.
- The number in the brackets “[]” next to each question are the marks allocated.
- Students must sign **IN** and **OUT** on the examination class list.
- Students must **not** write their names on their answer sheets, only their ID number
- Please number your responses accurately.


**DO NOT TURN THIS COVER SHEET UNTIL
YOU ARE TOLD TO DO SO!!!**

SECTION A


Answer ALL questions.

1. State the function of the following gates: AND, NOR and XOR [6]

 2. Determine the output waveform for the diagrams shown below [6]



 3. Determine the **Boolean Expression** for the following combinational logic circuit. [5]



4. Draw the **truth table** for the circuit diagram shown in question three (3) above. [6]

5. Draw the logic circuit for the following Boolean expression: [4]

$$Y = \overline{ABC} + \overline{D} + \overline{A\overline{B}} + \overline{BC}$$


6. Simplify the following Boolean expression using the rules and theorems of Boolean algebra: [4]

$$Y = \overline{ABC} + \overline{D} + \overline{A\overline{B}} + \overline{BC}$$

7. Use a Karnaugh map to simplify the following boolean expression: [8]

$$X = \overline{B}(C\overline{D} + \overline{A}D) + \overline{B}\overline{C}(A + \overline{A}\overline{D})$$

 8. Redraw the following circuit using NOR gates only [11]



Total [50 Marks]


SECTION B

Answer any two (2) questions.

Question One

(A) Draw the block diagram, truth table and circuit diagram for a half adder. [6]

 (B) Draw the output waveforms for the diagram shown below:




[4]

(C) Draw a 4 bit parallel adder using one half adder and three full adders. [3]

(D) Draw the circuit diagram for a full subtractor. [4]

 (E) Draw the output waveforms for the diagram shown below:




[3]

Question Two


(A) Draw logic circuits diagrams of the SR latch using NAND gates only and NOR gates only. [4]

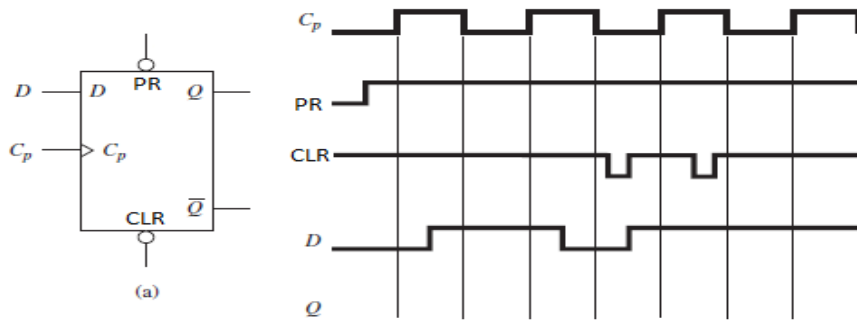(B) Draw the characteristics table for the device and the Q output for the diagram shown below.



[6]

 (C) Draw the Q and \bar{Q} outputs for the diagram shown below.




a. [4]

(D) Define the following terms: sequential logic circuit, asynchronous sequential logic circuit, synchronous sequential logic circuit [6]

Question Three

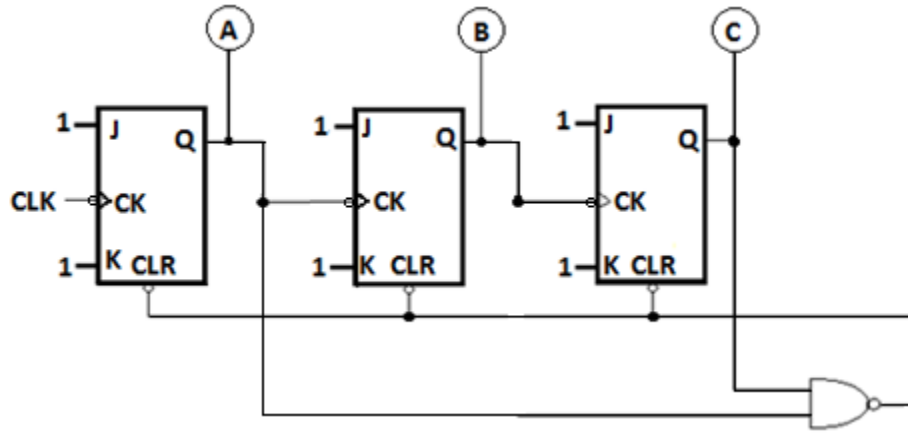- (A) Produce the output waveforms for the next eight (8) clock cycles. The initial state of outputs CBA is 011.



[4]

- (B) Give the four main characteristics of the device shown above. [4]
- (C) Produce a diagram of a three-bit register connected as SIPO. [3]
- (D) A four bit Johnson counter has the initial conditions 0101. Produce the next state table (truth table), for the next five clock cycles. [5]
- (E) Draw the circuit diagram for a 4-bit synchronous counter. [4]

Total [40 Marks]

END OF EXAMINATION!!