

SIR ARTHUR LEWIS COMMUNITY COLLEGE
FACULTY OF ENGINEERING
ACADEMIC YEAR (2024/2025) - SEMESTER TWO
END OF SEMESTER EXAMINATION

LECTURER (S) : Mr Arnaldo Sanchez Rojo
PROGRAMME : Electrical Engineering
COURSE TITLE : Electrical Principles II
COURSE CODE : ELT211
LEVEL : Associate Degree/ Year Twos
PAPER : One (1)
DATE : Monday, 5th May 2025
COMMENCEMENT TIME : 9:00a.m.
DURATION : Two (2) Hours
INVIGILATOR(S) : M. St. Clair (Chief) & K. Frederick
ROOM(S) : LFT-1R-02

GENERAL INFORMATION AND INSTRUCTIONS


- This paper consist of One (1) Section with five (5) long answer questions. You are required to answer all questions within this section. Marks are awarded accordingly.
- Students must produce sufficient working steps, to justify solution.
- Write legibly in blue or black ink. Please number your responses accurately.
- The number in the brackets “[]” next to each question are the marks allocated.
- Students must sign **IN** and **OUT** on the examination class list.
- Students must **not** write their names on their answer sheets, only their ID number
- **Calculators are needed.**

**DO NOT TURN THIS COVER SHEET UNTIL
YOU ARE TOLD TO DO SO!!!**

SECTION A

Answer all questions on the foolscap provided.

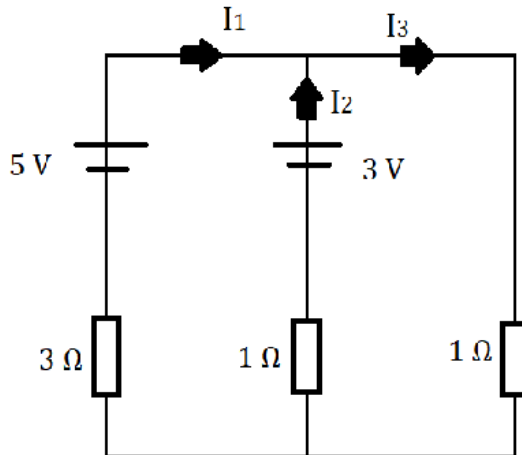1. Use Krichhoff's laws to determine the current flowing in each branch of the network shown in the figure. **[15 Marks]**



2. The winding of an electromagnet has an inductance of 15 H and a resistance of 30 Ω . When it is connected to a 120 V, d.c. supply, calculate:

- (A) the steady state value of current flowing in the winding,
- (B) the time constant of the circuit,
- (C) the value of the induced e.m.f. after 0.25 s,
- (D) the value of the current after 0.5 s

[20 Marks]

3. A coil of inductance 159.2 mH and resistance 10 Ω is connected in **series** with a 50 Ω resistor to a 120 V, 50 Hz supply. Determine:

- (A) the impedance of the circuit,
- (B) the current in the circuit,
- (C) the circuit phase angle
- (D) the p.d. across the 50 Ω resistor
- (E) the p.d. across the coil

[25 Marks]

4. A coil of inductance 100 mH and resistance 20 Ω is connected in **parallel** with a 40 μF capacitor across a 240 V, 50 Hz supply. Calculate:

- (A) the current in the coil and its phase angle
- (B) the current in the capacitor and its phase angle
- (C) the supply current and its phase angle
- (D) the circuit impedance
- (E) the power consumed
- (F) the apparent power
- (G) the reactive power.

[30 Marks]

5. A transformer has a primary winding of 2500 turns and a voltage of 480 V. If we want to get 120 volts in the secondary winding.

- (A) How many turns should the secondary winding has?
- (B) Classify the transformer in Step-up or Step-down transformer and explain your answer.

[10 Marks]

Total [100 Marks]

END OF EXAMINATION!!!