

SIR ARTHUR LEWIS COMMUNITY COLLEGE

FACULTY OF ENGINEERING

ACADEMIC YEAR (2024/2025) - SEMESTER TWO

END OF SEMESTER EXAMINATION

LECTURER(S) : **Mr Kwame Frederick**
PROGRAMME TITLE : **Mechanical Engineering**
COURSE TITLE : **Applied Electricity**
COURSE CODE : **ELT213**
LEVEL : **Associate degree**
PAPER : **Alternate**
DATE : **Monday, 26th May 2025**
COMMENCEMENT TIME : **9:00a.m.**
DURATION : **Two (2) Hours**
INVIGILATOR(S) : **-**
ROOM(S) : **VAR-02-02**
STUDENT ID :

GENERAL INFORMATION AND INSTRUCTIONS

- This paper contains **One (1) Section** with **five (5) questions**. You are required to answer **Three (3) Questions**. You must attempt **Question 4 and Question 5** (both are compulsory), and **one (1) question from Questions 1 to 3**.
- All questions must be attempted **on this question paper in the spaces provided**.
- Students must sign **IN** and **OUT** on the examination class list.
- Students must **not** write their names on their answer sheets, only their ID number.
- Students are reminded to read **all** questions and instructions in each section very carefully.
- Please number your responses accordingly.
- Where you are required to draw to scale **FREE HAND SKETCHES** will not be accepted.
- **Formula sheet can be found on the last page.**
- **Calculators are needed.**

**DO NOT TURN THIS COVER SHEET UNTIL
YOU ARE TOLD TO DO SO!!!**

SECTION A: Long Answer Questions

Answer Three (3) questions

(Questions 4 and 5 are compulsory) and one (1) question from Questions 1 to 3

Question 1


Two alternating currents flowing through parallel branches are given by:

$$i_1 = 15 \sin(\omega t) \text{ A}$$

$$i_2 = 10 \sin\left(\omega t + \frac{\pi}{6}\right) \text{ A}$$

- a) Sketch the waveforms of both currents over one cycle, showing maximum values and phase shift.
- b) Construct a phasor diagram to scale (1 cm = 5 A) and determine the resultant current.
- c) Express the resultant current in trigonometric form and calculate its r.m.s. value and frequency (assume 50 Hz supply).

[25 Marks]

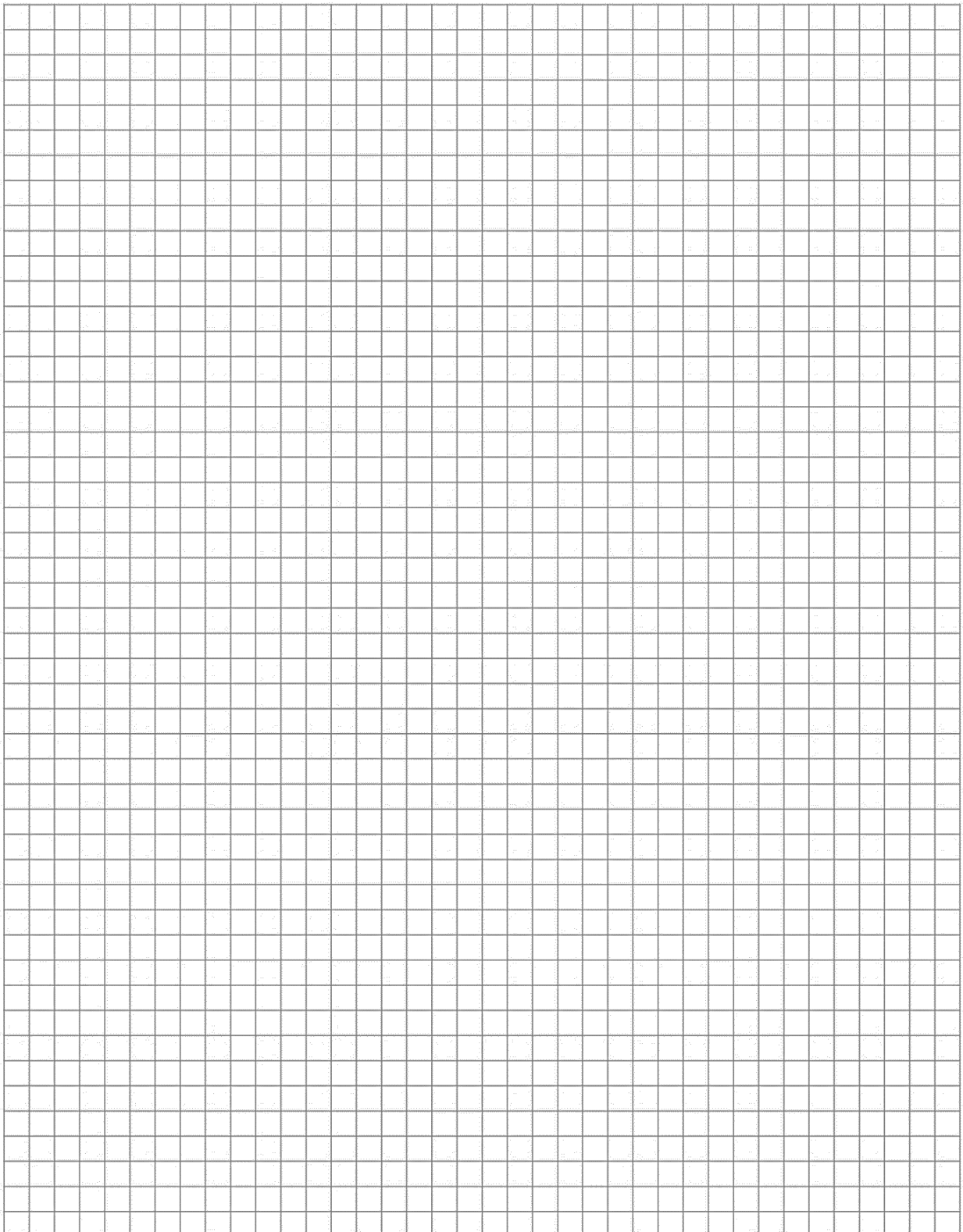

Student ID# _____

Show working below

Student ID# _____


Question 2

Four e.m.f.s are induced in series-connected coils as follows:

$$E_1 = 12\angle 0^\circ \text{ V}, E_2 = 9\angle 90^\circ \text{ V}, E_3 = 7\angle 180^\circ \text{ V}, E_4 = 10\angle 270^\circ \text{ V}$$

- a) Draw a scaled phasor diagram (1 cm = 3 V) showing all e.m.f.s.
- b) Calculate the total resultant e.m.f.
- c) Find the phase difference between the resultant and (i) E_2 , (ii) E_3 .

[25 Marks]

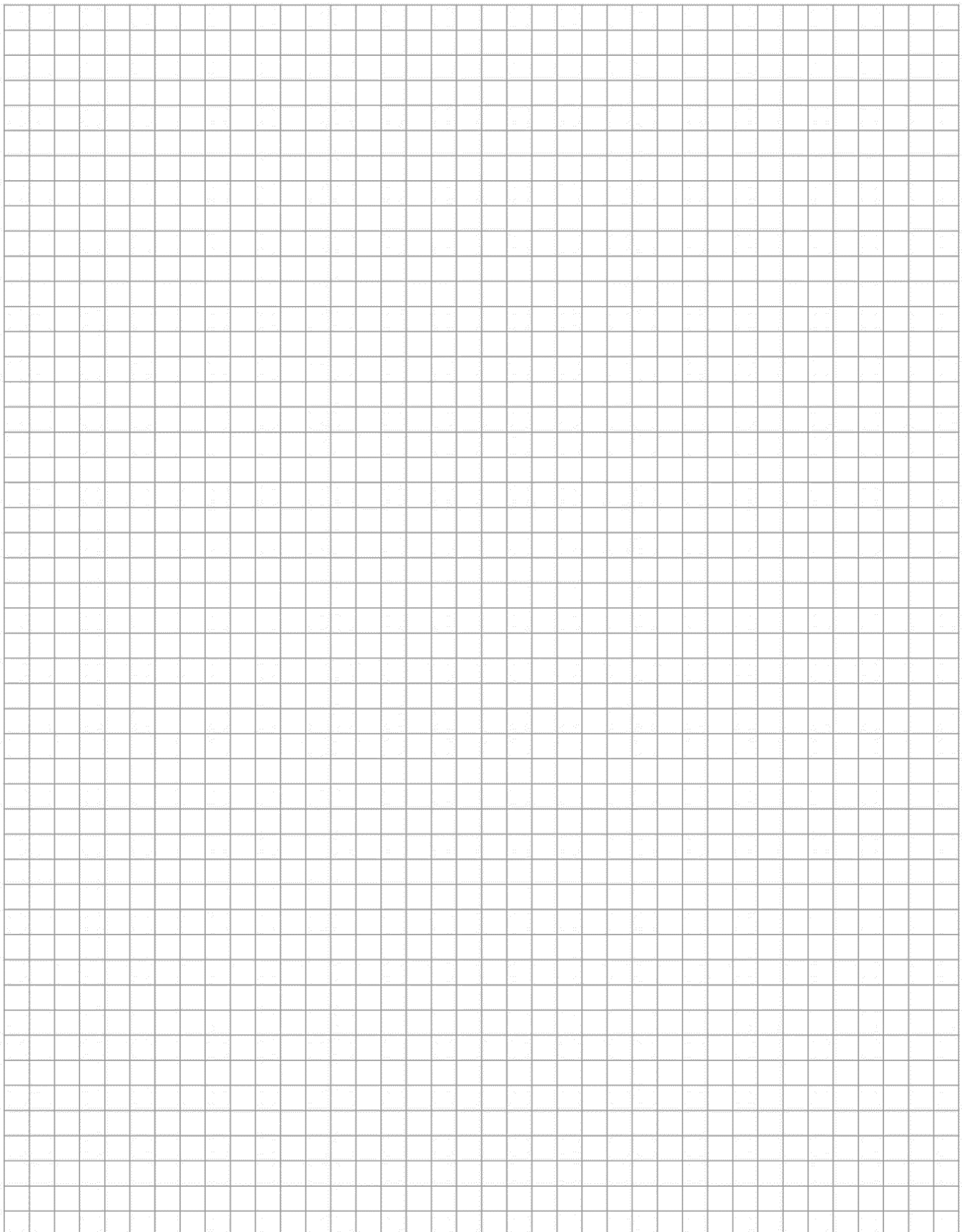

Student ID# _____

Show working below

Question 3

A single-phase circuit consists of three parallel branches with the following current contributions:?


Branch A: $12\angle 0^\circ A$

Branch B: $6\angle -60^\circ A$

Branch C: $5\angle +90^\circ A$

- a) Draw a phasor diagram (1 cm = 2 A) showing all branch currents.
- b) Calculate the total current taken from the supply and its phase angle.
- c) Express the total current in polar and rectangular forms.
- d) If the supply voltage is $V=220V$, calculate the total impedance, resistance, and reactance.

[25 marks]

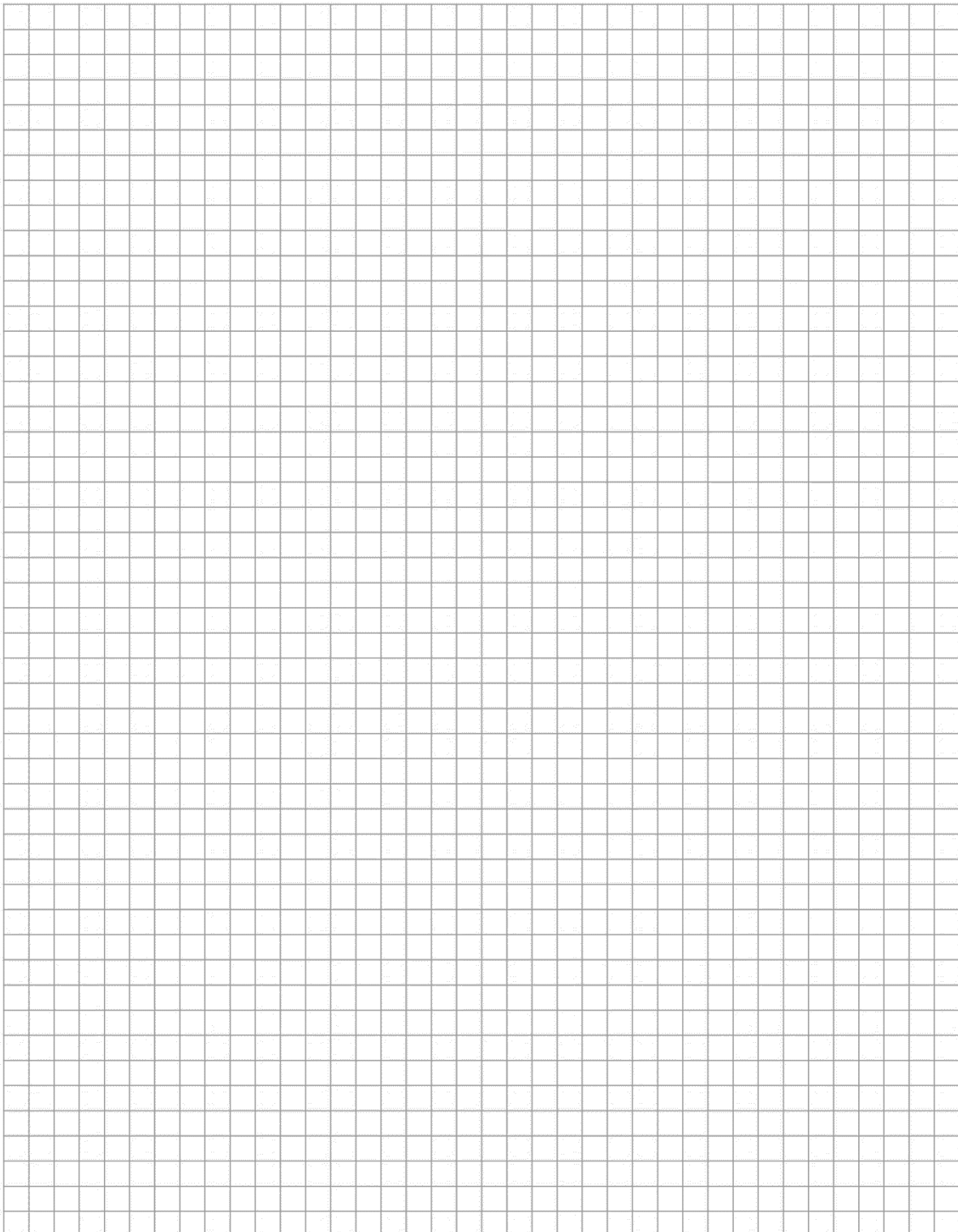

Student ID# _____

Show working below

Student ID# _____

Question 4

A 240 V single-phase supply feeds the following:

1. A water heater drawing 10 A at unity power factor.
2. An air conditioner drawing 6 A at 0.85 lagging power factor.
3. A solar inverter feeding back 4 A at 0.95 leading power factor.

- a) Construct a phasor diagram showing all current components.
- b) Determine the total supply current, active power, reactive power, and overall power factor.

[25 Marks]

Student ID# _____

Show working below

Total [90 Marks]

END OF EXAMINATION!!!

FORMULA SHEET

General AC Theory

Trigonometric current/voltage form: $i(t) = I_m \sin(\omega t + \phi)$

RMS value: $I_{rms} = \frac{I_{max}}{\sqrt{2}}$

Frequency and angular frequency: $\omega = 2\pi f$

Phasor Addition & Resultant

Phasor representation: $I = I \angle \theta$

Resultant current (phasor sum): $I_{res} = \sqrt{(I_x)^2 + (I_y)^2}$

Phase angle of resultant: $\theta = \tan^{-1} \left(\frac{I_y}{I_x} \right)$

Power in AC Circuits

Active Power (Real Power): $P = VI \cos \phi$

Reactive Power: $Q = VI \sin \phi$

Apparent Power: $S = VI$ or $S = \sqrt{P^2 + Q^2}$

Power Factor: $pf = \cos \phi = \frac{P}{S}$

Impedance and Power Factor (Single-phase)

Impedance: $Z = \frac{V}{I}$

Impedance components: $Z = R + jX$ where $|Z| = \sqrt{R^2 + X^2}$

Power factor from impedance: $\cos \phi = \frac{R}{|Z|}$

Three-Phase System

Line and phase voltage (Delta or Star connection):

Delta: $V_L = V_\phi, I_L = \sqrt{3}I_\phi$

Star: $V_L = \sqrt{3}V_\phi, I_L = I_\phi$

Power per phase: $P = V_\phi I_\phi \cos \phi, Q = V_\phi I_\phi \sin \phi, S = V_\phi I_\phi$

Vector Calculations

Rectangular to polar conversion: $r = \sqrt{x^2 + y^2}, \theta = \tan^{-1} \left(\frac{y}{x} \right)$

Polar to rectangular conversion: $x = r \cos \theta, y = r \sin \theta$