



**SIR ARTHUR LEWIS COMMUNITY COLLEGE
ACADEMIC YEAR (2024/2025) – SEMESTER TWO
END OF SEMESTER FINAL EXAMINATION**

***COURSE CODE* : PHY218**

***COURSE TITLE* : Electricity, Electronics and Modern Physics**

***LECTURER(S)* : MR CECIL FEVRIER**

***DATE* : May 8, 2025**

***TIME* : 1 p.m.**

***DURATION* : 2 HOURS**

***STUDENT ID #* : _____**



GENERAL INFORMATION AND INSTRUCTIONS

- Students must sign **IN** and **OUT** on the examination class list.
- Write your ID number on the question paper.
- This paper has seven (7) structured questions, in **THREE** sections.
- Answer a total of five (5) questions.
- You must answer at least **ONE** question from each section.

DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO

Instructions: This paper has seven (7) structured questions, in THREE sections.

Answer a total of five (5) questions.

You must answer at least ONE question from each section.

Section A

1.
- (a)

(i)

Distinguish between a digital system and an analog system.

[2]

(ii)

Explain one advantage of using digital systems over analog systems.

[2]
- (b)

What logic function is equivalent to two switches connected in series?

[1]
- (c)

The logic circuit in Figure 1 uses four identical logic gates to perform a logic function.

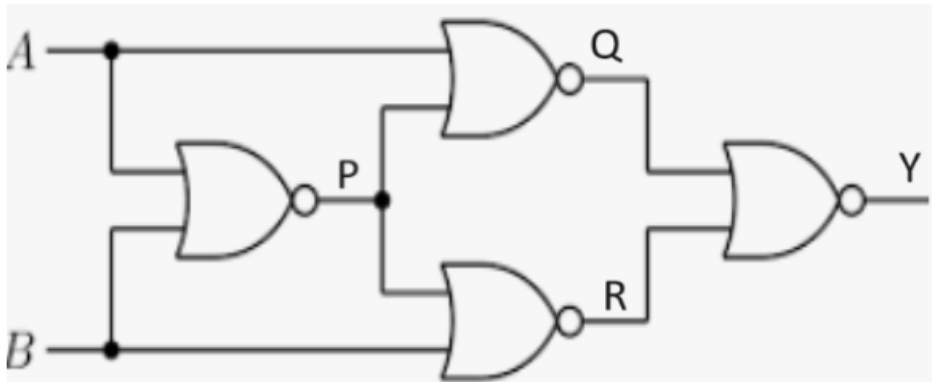


Figure 1

- (i)

What is the name of the logic gates used in the circuit?

[1]
- (ii)

Draw the truth table for the logic circuit.

[4]
- (iii)

Use the truth table to determine the equivalent gate of the circuit.

[2]

2.

(a)

State THREE characteristics of the ideal operational amplifier and their Implications for the ideal operational amplifier.

[3]

(b)

What effect does negative feedback have on the gain and bandwidth of an operational amplifier?

[2]

(c)

Figure 2 shows two circuits A and B cascaded to produce an output, V_o .

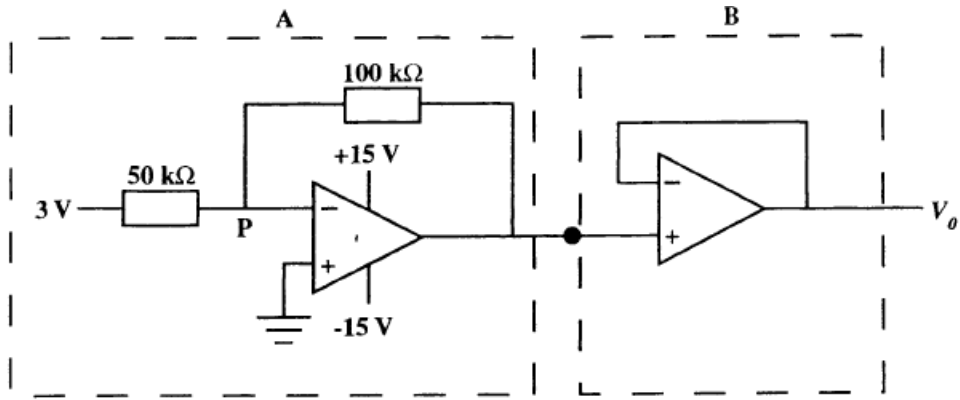


Figure 2

- (i)

Identify the type of amplifier used in circuit A and circuit B.

[2]
- (ii)

Determine the output voltage, V_o , of the circuit.

[4]
- (iii)

Suggest a practical use for circuit B.

[1]

3. (a) What are the main characteristics of an operational amplifier (OP AMP)? [2]
- (b) Op amps are widely used in electronics to perform a number of functions. They are often used as inverting amplifiers and non-inverting amplifiers.
- (i) Identify one feature that the two amplifier circuits have in common. [1]
- (ii) Determine the output voltage of the circuit shown in Figure 2 (a) for a sinusoidal input of 2.5 mV

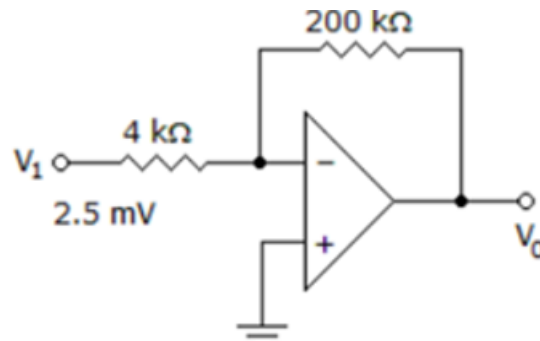


Figure 2 (a)

[4]

- (c) A comparator circuit shown in Figure 2 (b) below is used to indicate temperature change.

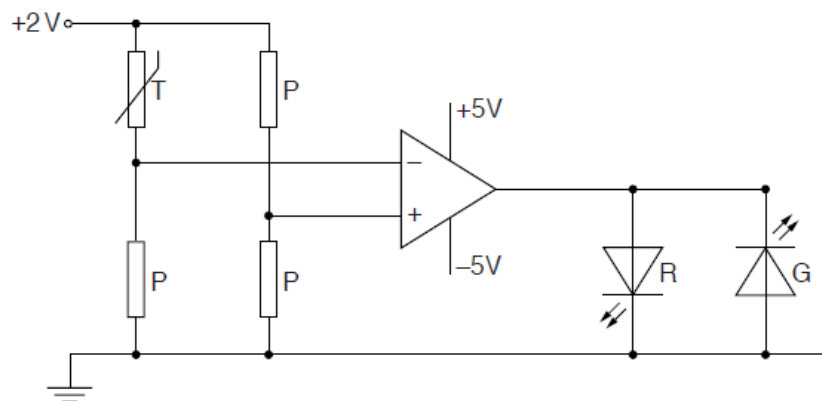


Figure 2 (b)

The resistance of the thermistor T is 2100 Ω at 16 $^{\circ}\text{C}$ and 1900 Ω at 18 $^{\circ}\text{C}$,
Each resistor P has a resistance of 2000 Ω .

- (i) Find the potential at the non-inverting terminal of the op-amp. [1]
- (ii) Find the potential at the inverting terminal when the temperature is 16 $^{\circ}\text{C}$. [2]
- (iii) Use your answers from (i) and (ii) to determine which LED would be on at 16 $^{\circ}\text{C}$. [2]

SECTION B

4. Figure 3 shows how an alternating current changes with time.

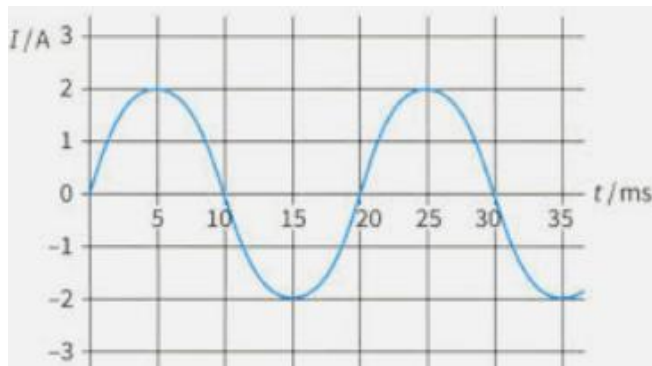


Figure 3

- (a) Find: (i) the peak to peak current, [2]
 (ii) the r.m.s. current, [2]
 (iii) the frequency of the current. [2]
- (b) In Figure 5, the battery's e.m.f. is 24.0 V, the total resistance is $2.0\text{ k}\Omega$ and the capacitance is $15\text{ }\mu\text{F}$.
- (i) What is the time constant of the circuit? [2]

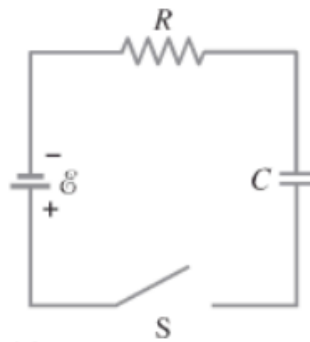


Figure 5

- (ii) Calculate the time it would take for the voltage across the resistor to fall to 12.0 V. [4]
5. (a) State Gauss' Law in words and write its mathematical form. Explain the physical significance of each term in the equation. [4]
- (b) A uniformly charged solid sphere of radius R carries a total charge Q . Use Gauss' Law to derive the electric field at a distance r from the center of the sphere, where:
- (i) $r < R$ (inside the sphere), [4]
 (ii) $r \geq R$ (outside the sphere). [4]

SECTION C

6. (a) What are the two postulates in Einstein's Special Theory of Relativity? [4]
- (b) What is meant by a proper length in terms of special relativity theory? [2]
- (c) A spaceship 100 m long and 30 m wide travels past the Earth at a speed of 0.95 c. What would be the length and width of the spaceship as measured by an observer on Earth? [4]
- (d) Find the rest energy of a proton, given that its mass is 1.67×10^{-27} kg. [2]
7. (a) Explain briefly Bohr's model of the hydrogen atom. [3]
- (b) Briefly describe and explain the formation of the emission spectra of hydrogen.[3]
- (c) Outline the two main differences between the Lyman and Balmer series in the hydrogen emission spectrum. [2]
- (d) The energy level of electrons in the ground state ($n=1$) of hydrogen gas is - 13.6 eV. How much energy is released when an electron moves from energy level 4 to energy level 2? [4]

END OF EXAMINATION